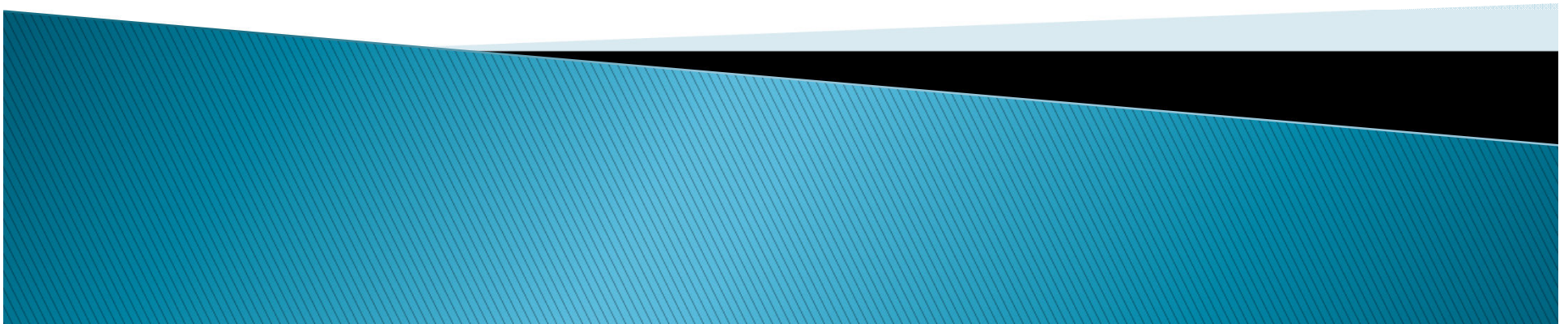


Analyzing the HR360WB Antenna Analyzer

By Barry Basile KG5IRR
For the Oak Forest Amateur Radio Club
11/18/17



Agenda

- ▶ What does it do?
- ▶ Original Design Proposal
- ▶ Understanding the SWR Bridge
- ▶ Understanding Diode Characteristics
- ▶ Simulations with Different Diodes
- ▶ Reverse Engineering – Specs
- ▶ Alternative Designs
- ▶ Future Plans



Objective

- ▶ Measure antenna system SWR and adjust system to achieve SWR near “1”
- ▶ Best for transmitter health
- ▶ Best efficiency (highest radiation)




Instrument Comparisons


- ▶ Objective: Measure Antenna System SWR


Instrument	Has Generator?	Frequency Sweep?	Measures Complex Impedance?	S Parameters
SWR Meter	No	No	No	No
Antenna Analyzer	Yes	Yes	No	No
Vector Network Analyzer (VNA)	Yes	Yes	Yes	Yes

Analyzer Block Diagram

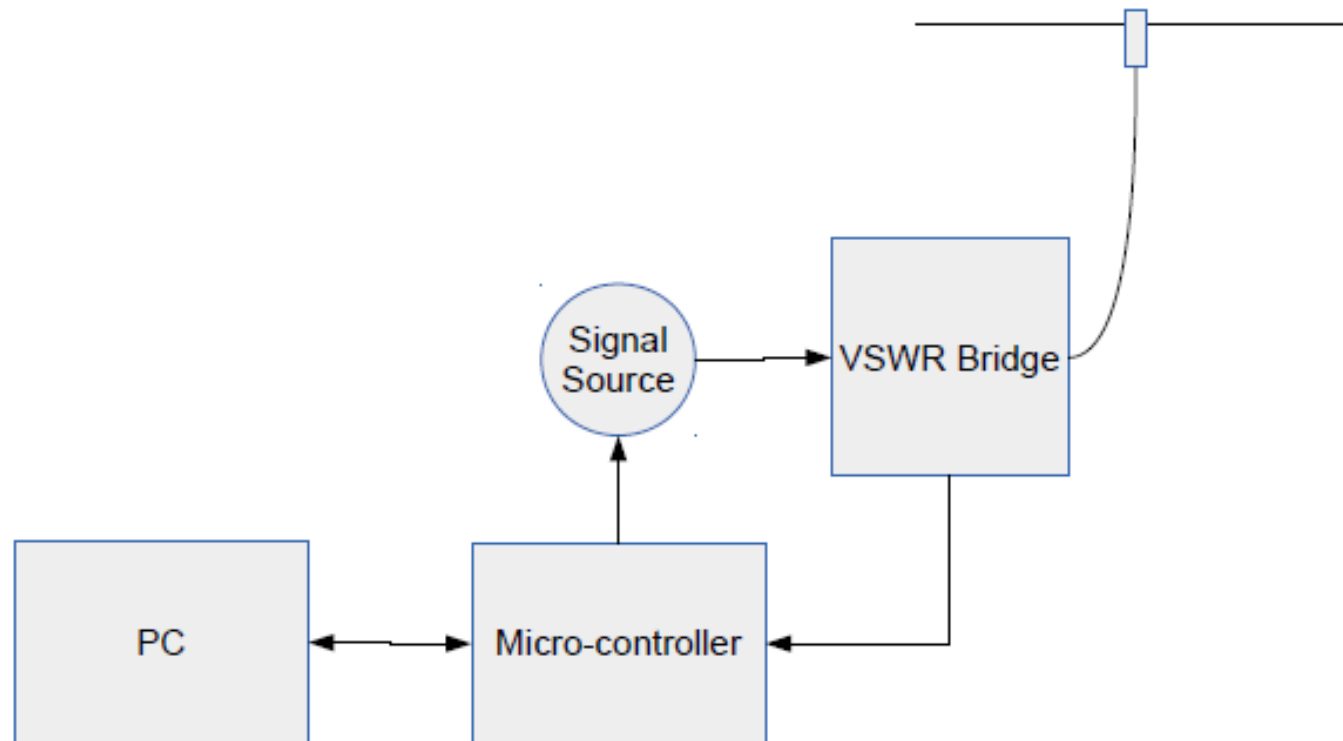

Finished Product

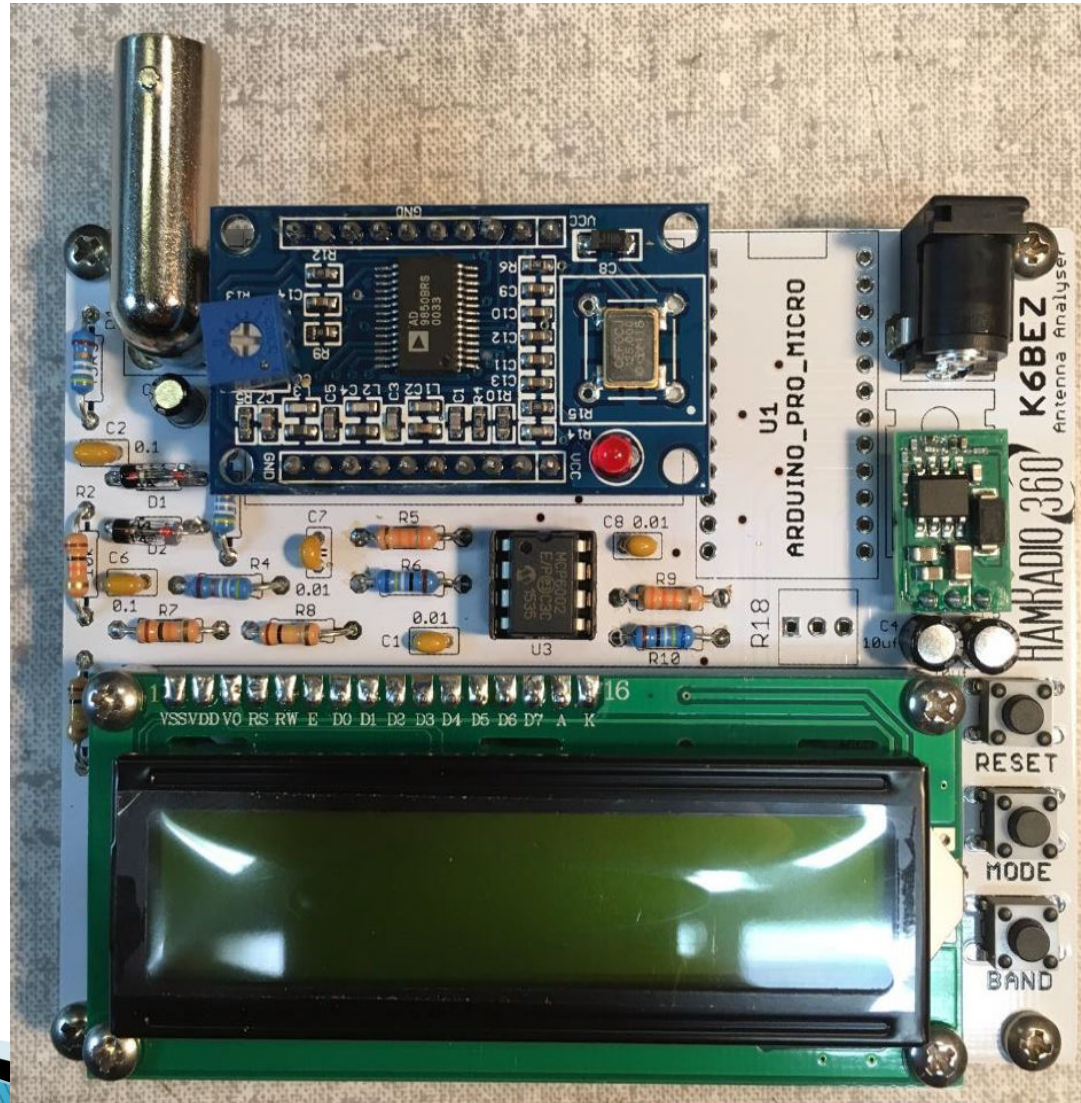

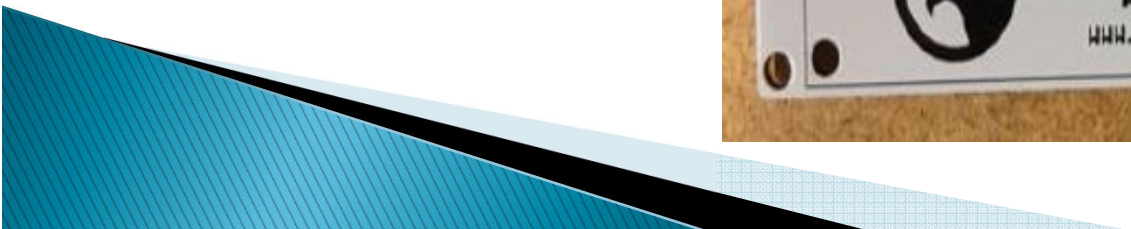

VSWR Theory

- ▶ VSWR is the ratio of maximum to minimum voltage seen along a length of antenna feedline.
- ▶ VSWR can be predicted if the characteristic impedance (Z_0) and the impedance of the (antenna) load are known.
- ▶ VSWR is defined by these equations:

$$\Gamma = (Z_L - Z_0) / (Z_L + Z_0)$$

$$\rho = |\Gamma|$$

$$\text{VSWR} = (1 + \rho) / (1 - \rho)$$






Analysis Tools / Resources


- ▶ Ham Radio 360 Work Bench web page
- ▶ Other web resources
- ▶ Project description from Beric Dunn K6BEZ
- ▶ TI SPICE analysis program (TINA)
- ▶ Microsoft Excel




VSWR Bridge Schematic

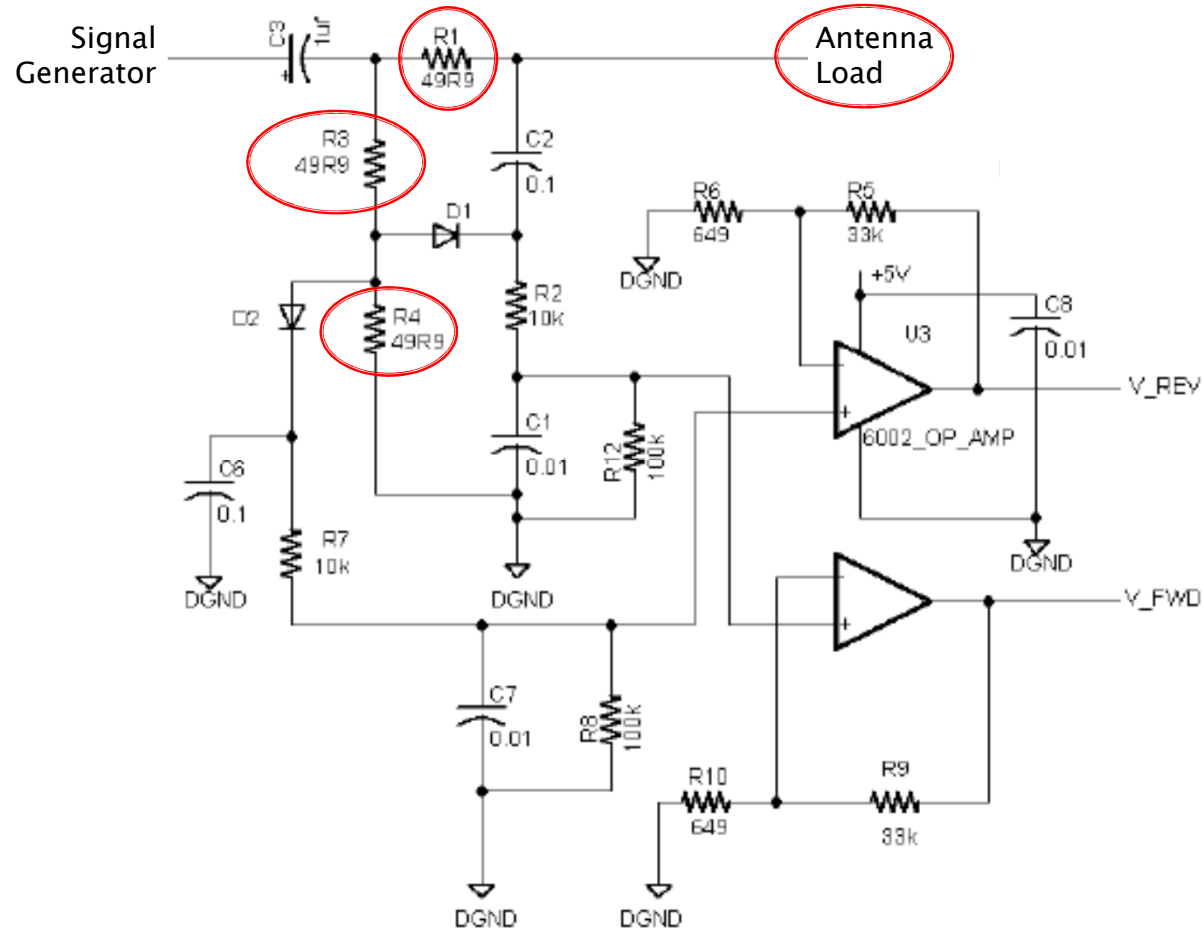

The Wheatstone Bridge

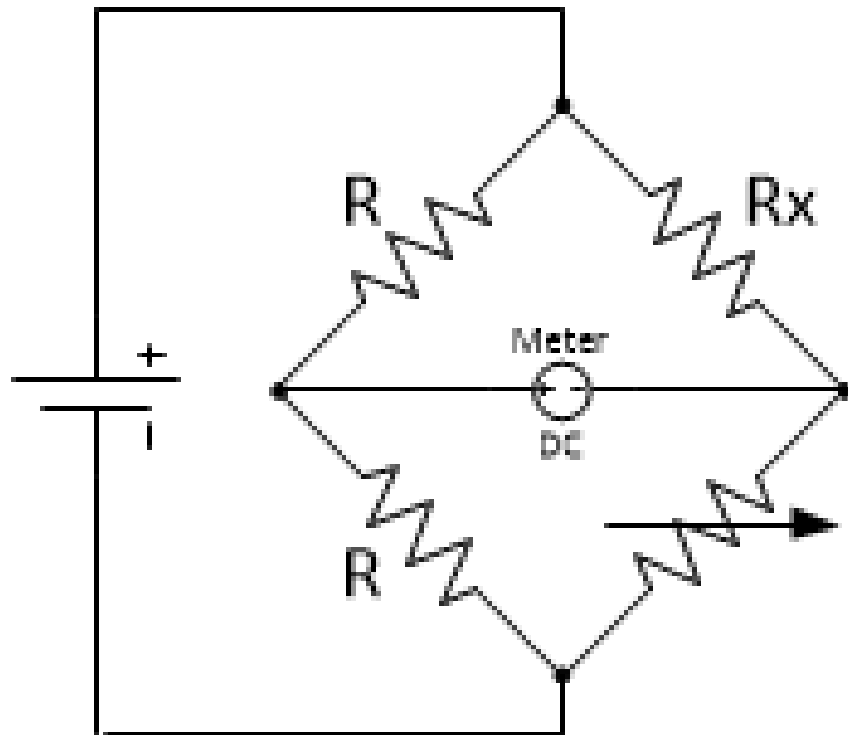

The VSWR Bridge

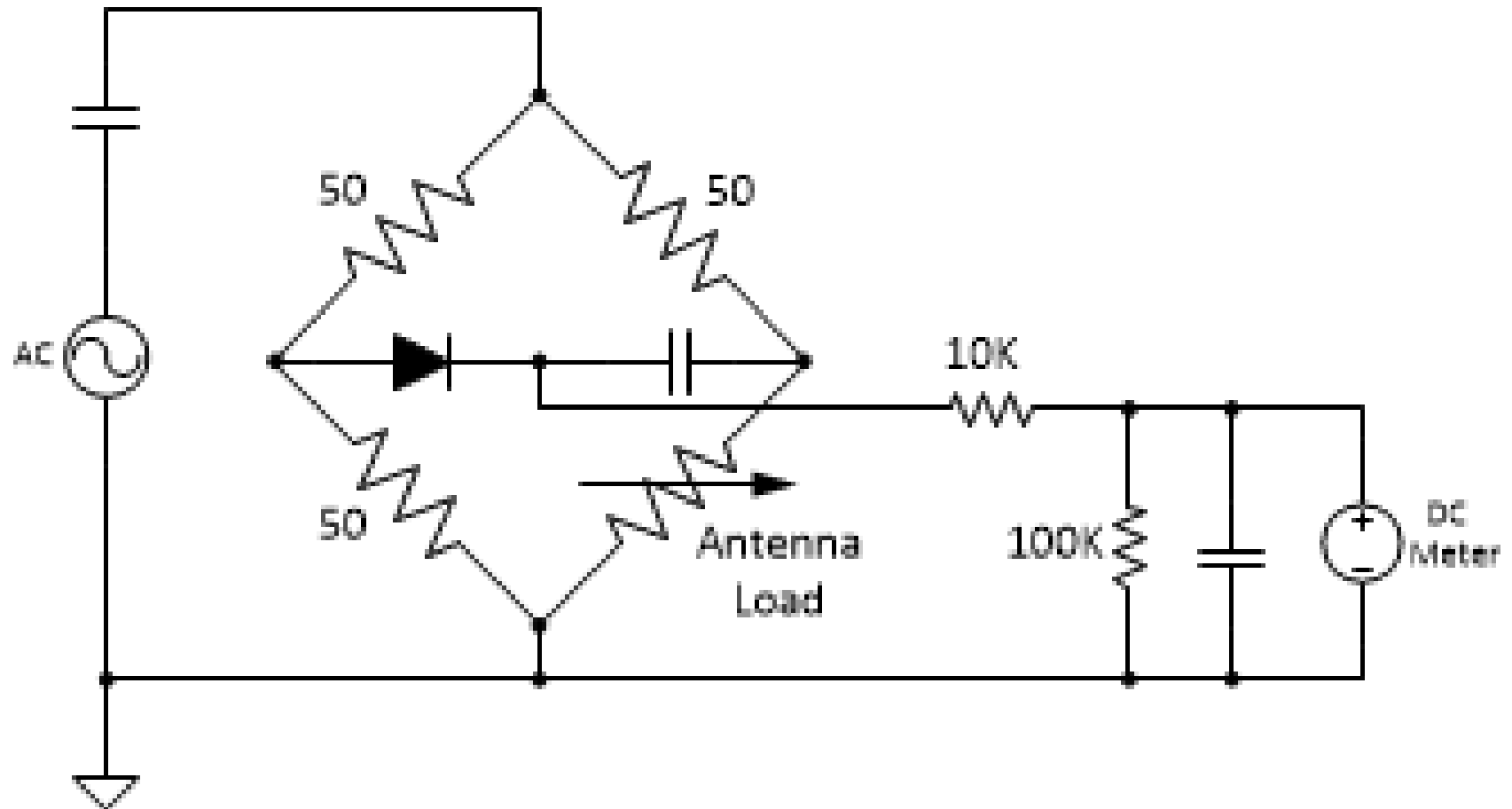

Magic Sauce – Detector Diode

- ▶ AA143 – no longer in production
- ▶ Is nearly unobtainium
- ▶ What makes it special?
 - Low forward voltage drop
 - Low conduction current
 - Low capacitance
 - Fast transfer time (high frequency)



Diodes – various packages



Diode Comparisons

Type	Example P/N	$V_F @ 1 \text{ ma}$	$I_R @ 20V$	T_{RR}	C_J	Junction
Silicon	1N914	0.62 V	0.025 μA	4 ns	4 pf	P-N
Germanium	1N34A AA143	0.3 V	25 μA	70 ns	0.5 pf	P-N
Schottky Barrier	1N5819 BAT17	0.5 V	0.1 μA	50 ns	1.5 pf	N-Metal
Ideal		0 V	0 μA	0 ns	0 pf	

SPICE


Diode Model Parameters

Silicon	Germanium	Schottky	Ideal	Parameter
1N914	!N34A	1N5819		Part Number
1E-9	1E-06	2E-07	1E-07	IS – controls forward and reverse current against voltage.
1.7	0.537	0.850	1E-07	N – controls forward current against voltage.
100	40	75	100	BV, IBV – control reverse breakdown characteristics.
4E-12	1.36E-10	5E-13	1E-14	CJO, M , VJ – control variation of capacitance with voltage.
1.11	1.11	0.670	1E-01	EG – controls barrier height.
0.002	0.0556	7	1E-03	RS – series resistance controls forward voltage at high current.
25.9E-9	1.67E-09	1E-10	1E-13	TT – controls switching reverse recovery characteristics.
10		10		RZ – zener Resistance


Diode Simulations – 50Ω Load

Barry Basile, 11/04/17
Diode DC Transfer Characteristics

1N4150, 1N5819, 1N34A, IDEAL

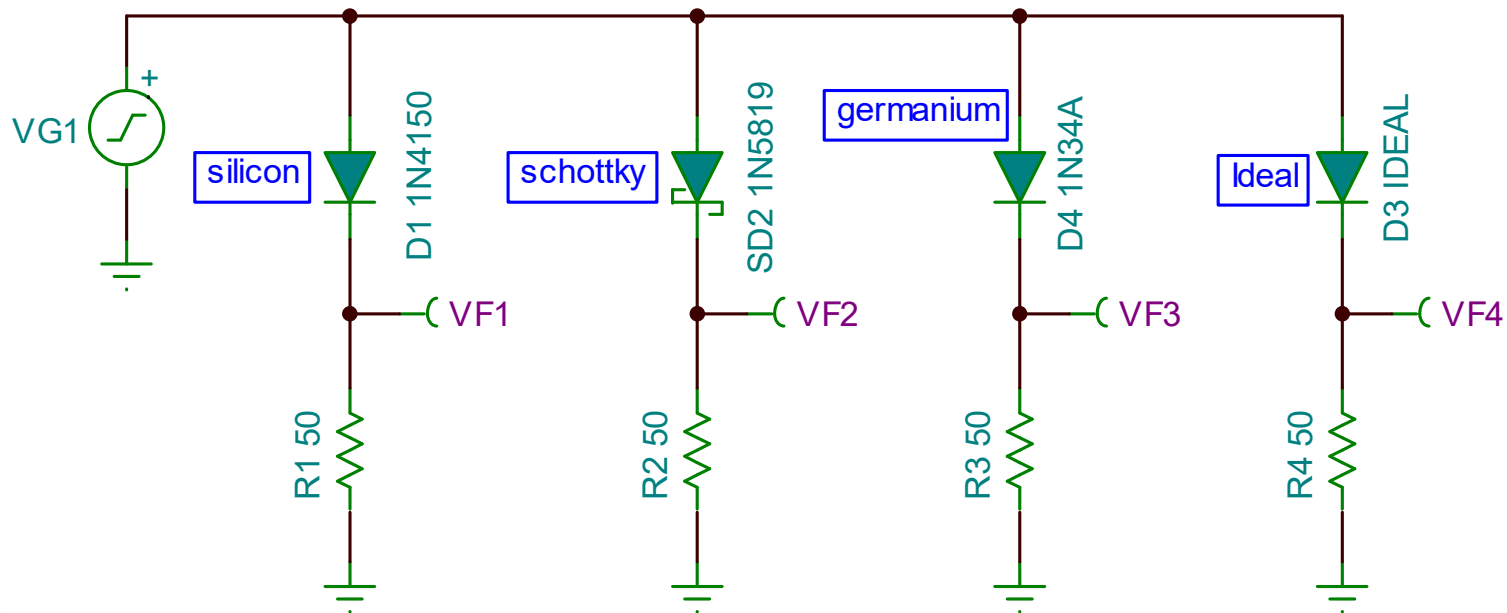

Voltage Transfer, 50Ω Load

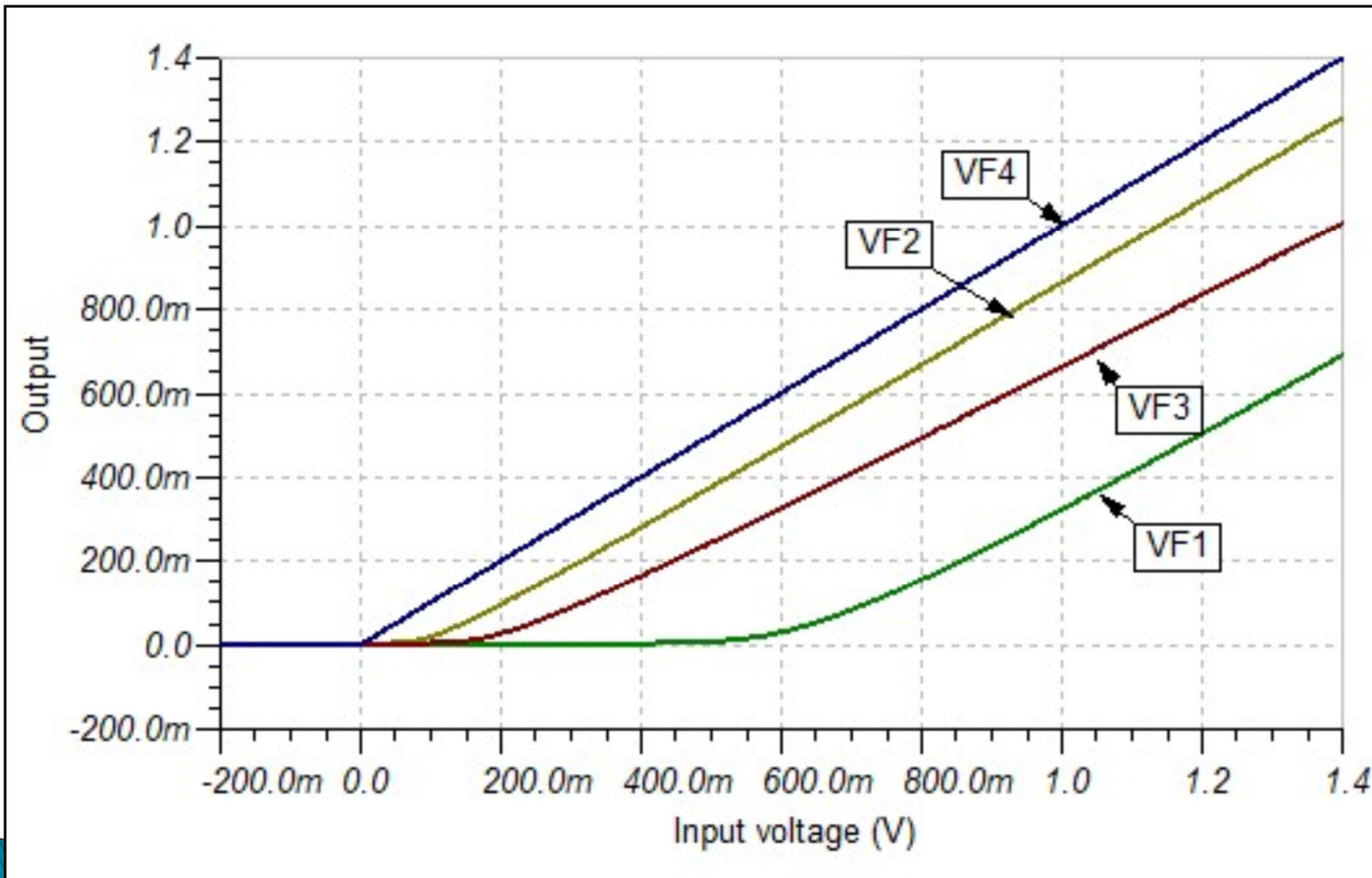


Diode Simulations – 100k Load


Barry Basile, 11/04/17

Diode DC Transfer Characteristics

1N4150, 1N5819, 1N34A, IDEAL

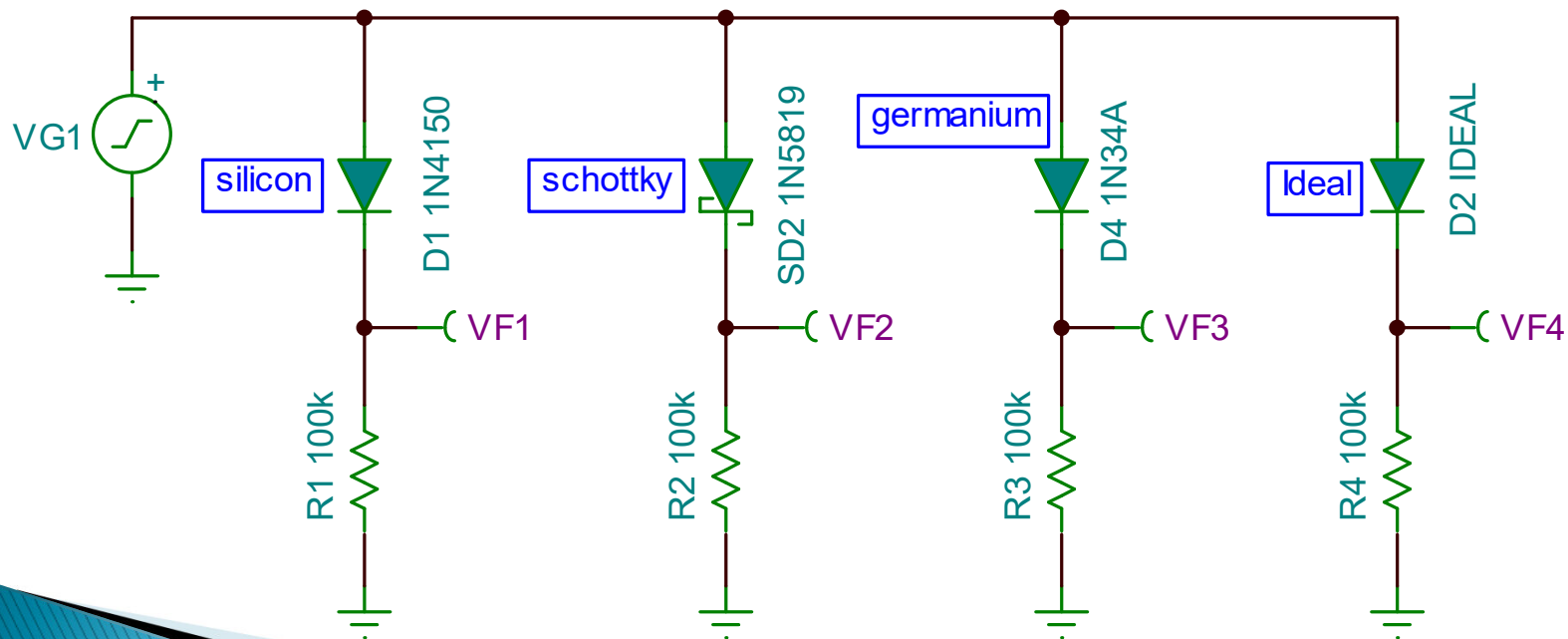

Voltage Transfer, $R_L = 100k$

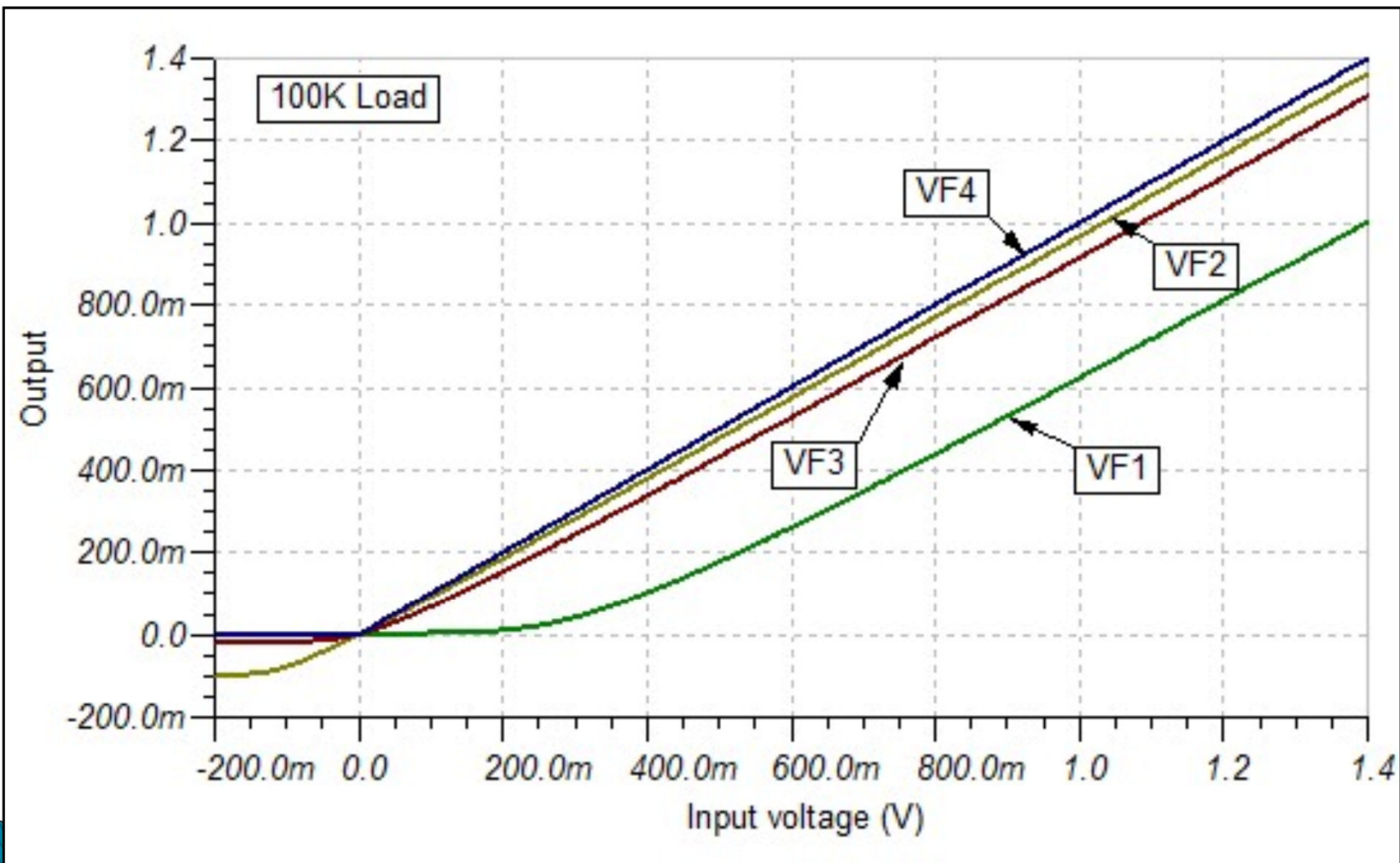

Reverse Engineering

ADC Voltage Range	0 – 5V	Assume 0–4V
Op amp Gain	$1 + R_F/R_I$	$1 + (33k/649) \sim 52$
VSWR Gain	0.5 – diode VF	Assume 0.4
DDS Output (sine)	$(4/52) / .4$	Assume about 200mv peak

MCU Code – Frequency Sweep

```
// Start loop
for(long i=0;i<=num_steps;i++){
    // Calculate current frequency
    current_freq = Fstart + i*Fstep;

    // Set DDS to current frequency
    SetDDSFreq(current_freq);
    // Wait a little for settling
    if(digitalRead(BAND) == LOW){mode_pressed=1;}
    delay(10); // 10 msec
    // Read the forward and reverse voltages
    REV = analogRead(A0);
    FWD = analogRead(A1);
```

MCU Code – VSWR Calculation

```
if (REV >= FWD) {  
    // To avoid a divide by zero or negative VSWR then set to max 999  
    VSWR = 999;  
} else {  
    // Calculate VSWR  
    VSWR = ((double) FWD + (double) REV) / ((double) FWD - (double) REV);  
}
```


// That is: $VSWR = (FWD + REV) / (FWD - REV)$;




Bridge Simulation – Ideal Diode

Barry Basile, 11/10/17


Wheatstone Bridge - ideal diode

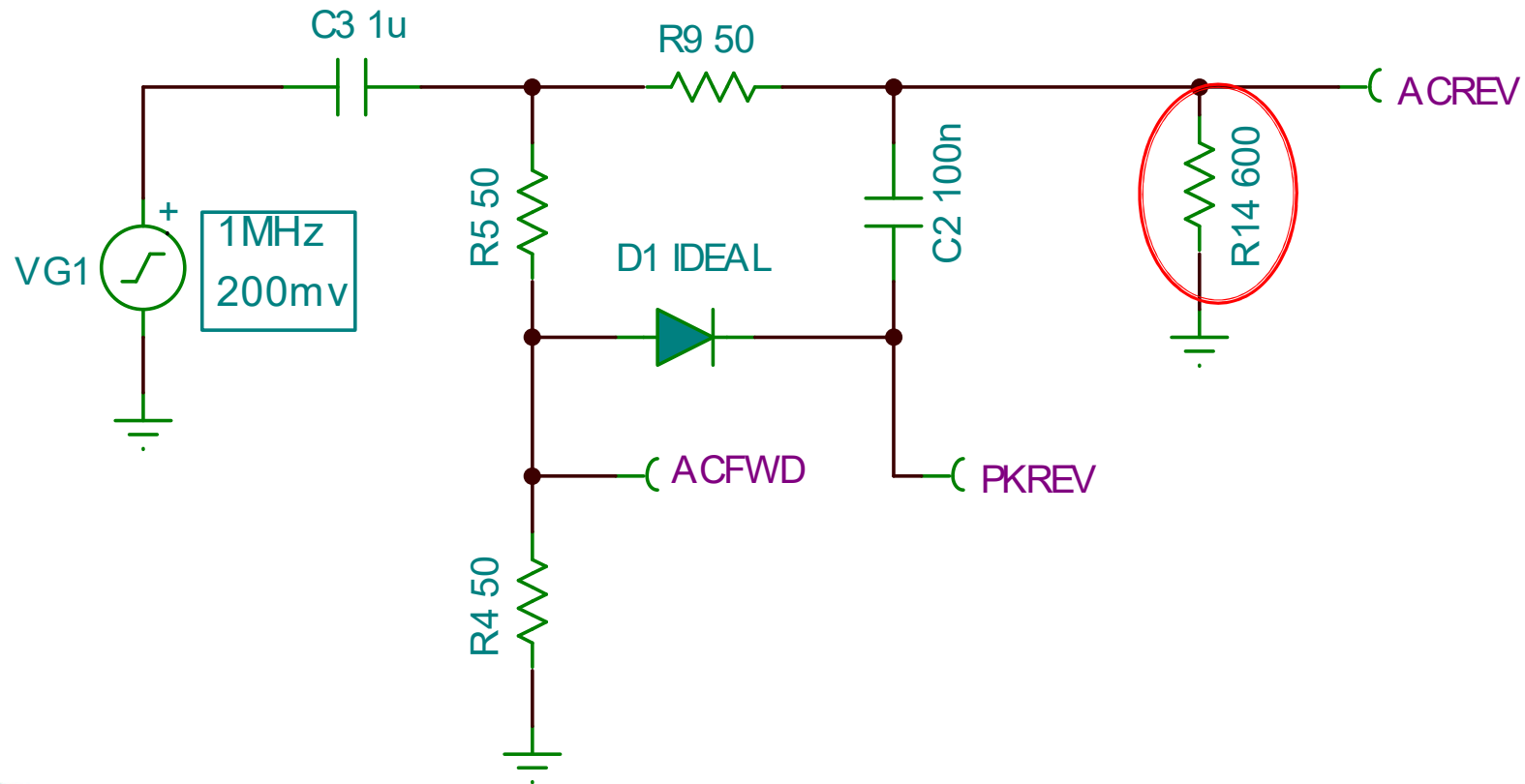


Simulation at $RL = 600\Omega$

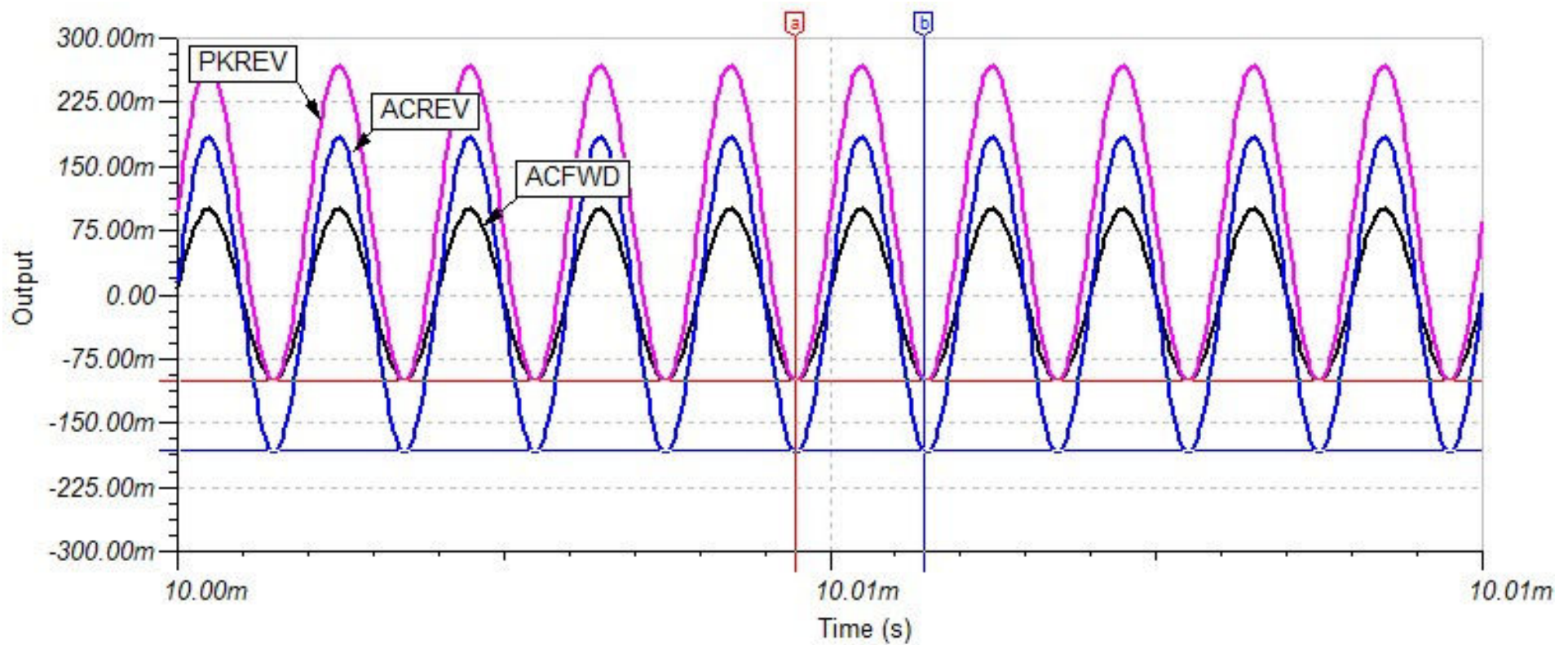


Simulation at $RL = 4\Omega$

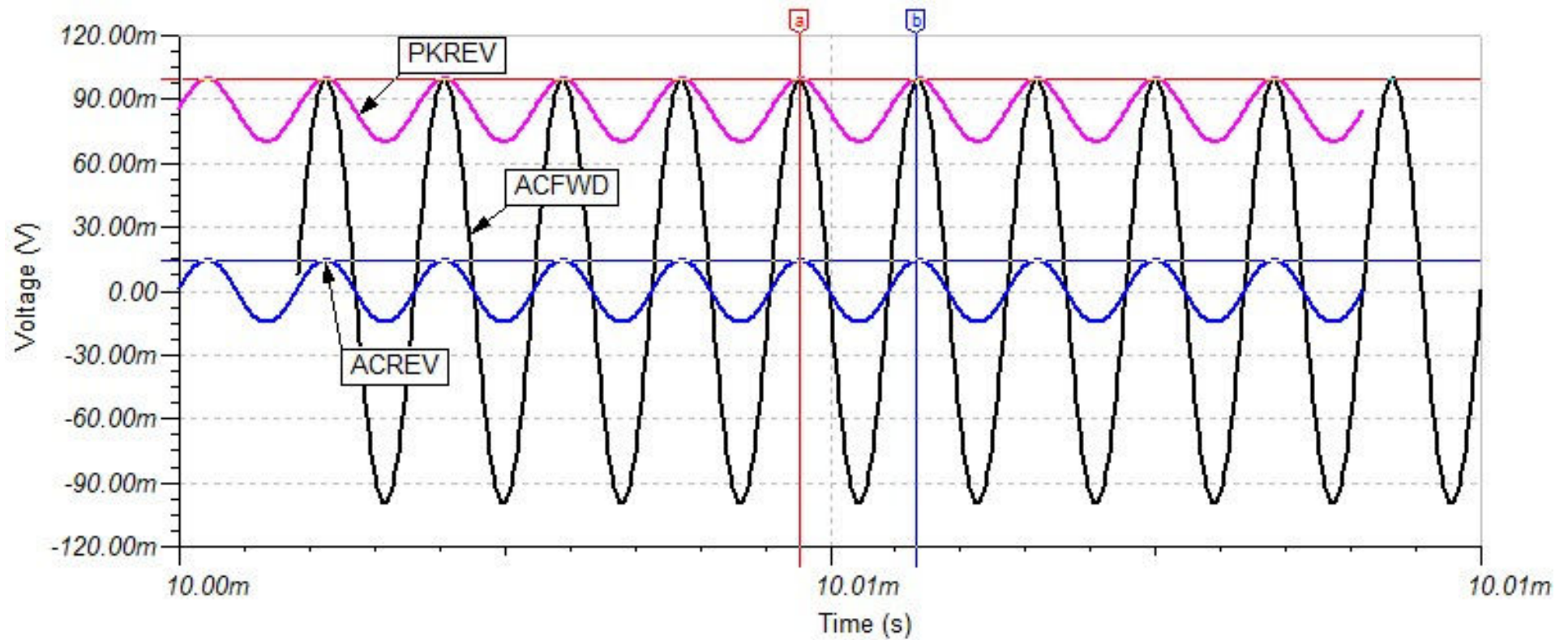


Forward Voltage – Reference

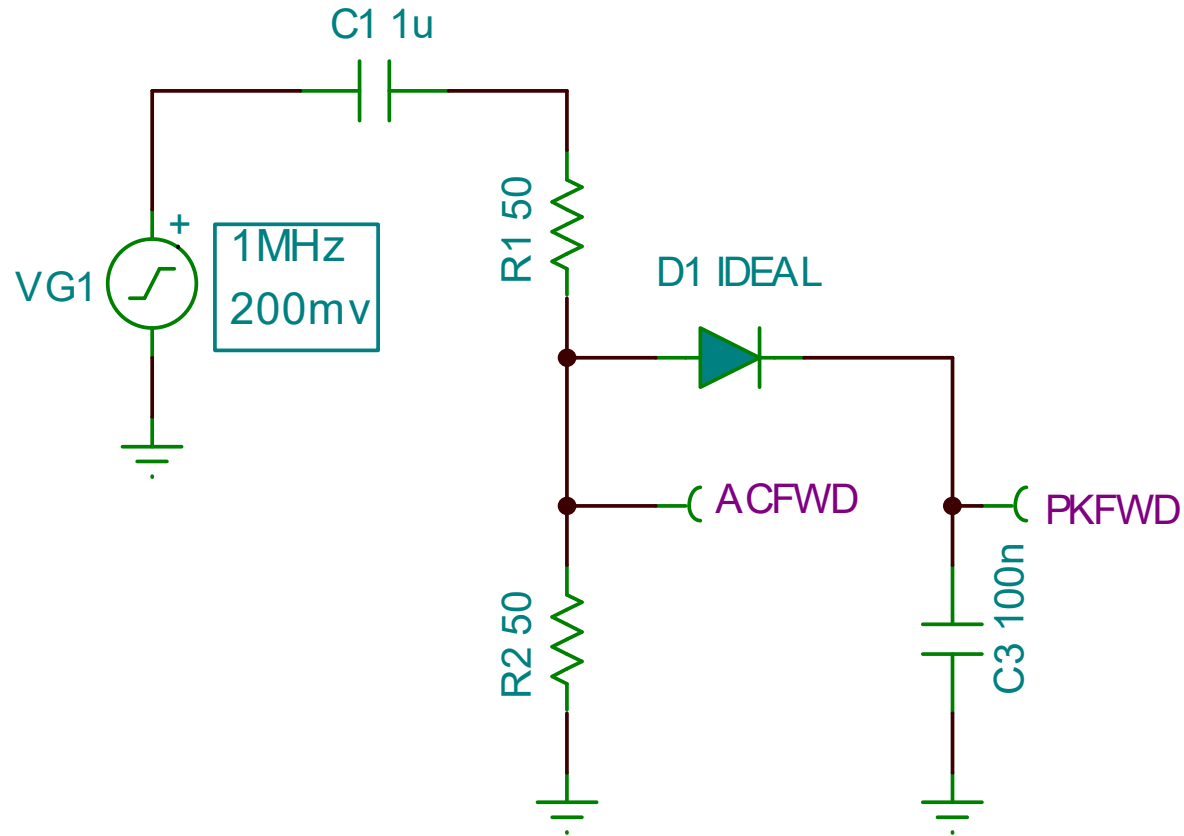


Forward Voltage Peak Detector

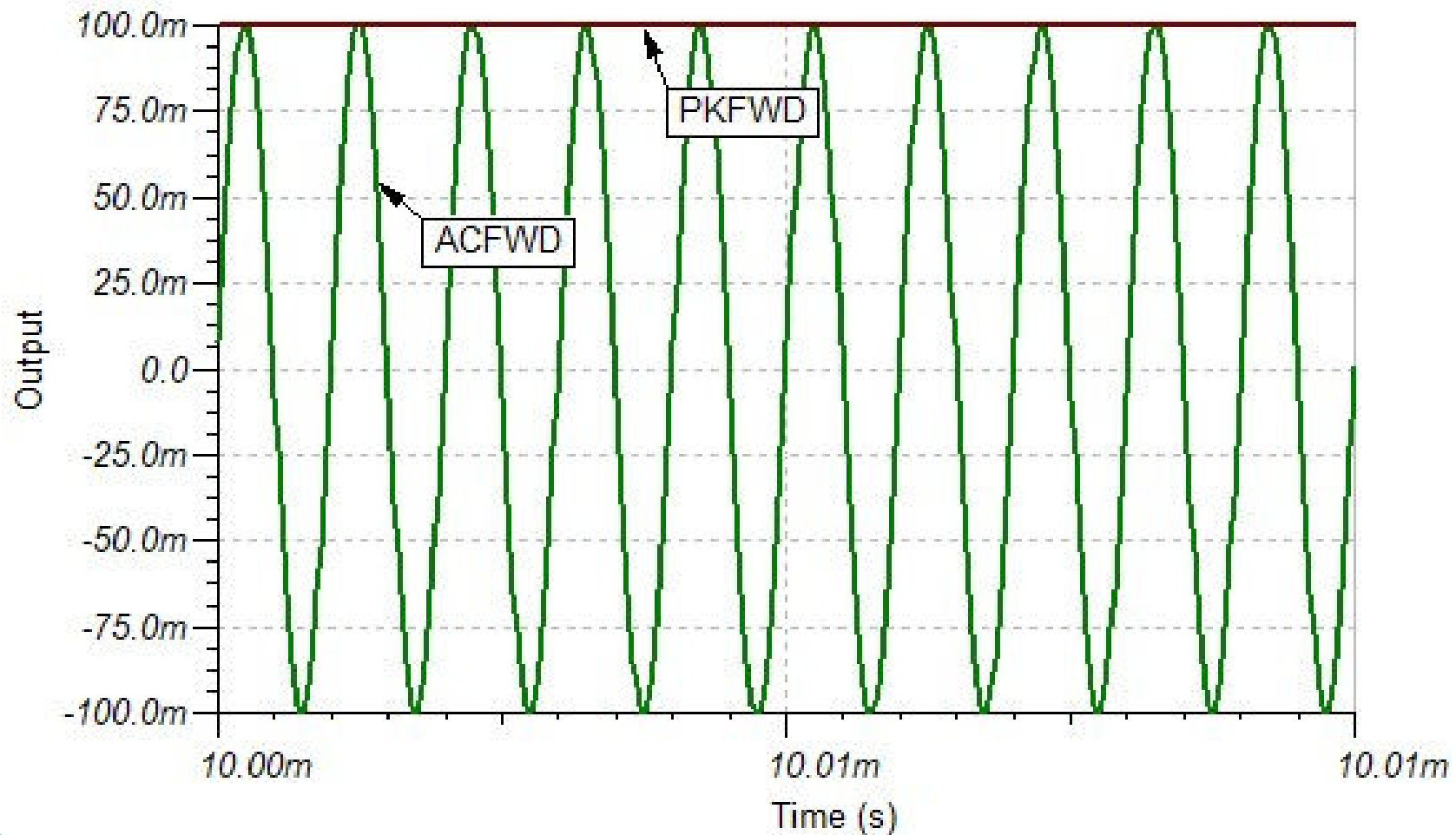

Simulation Circuit

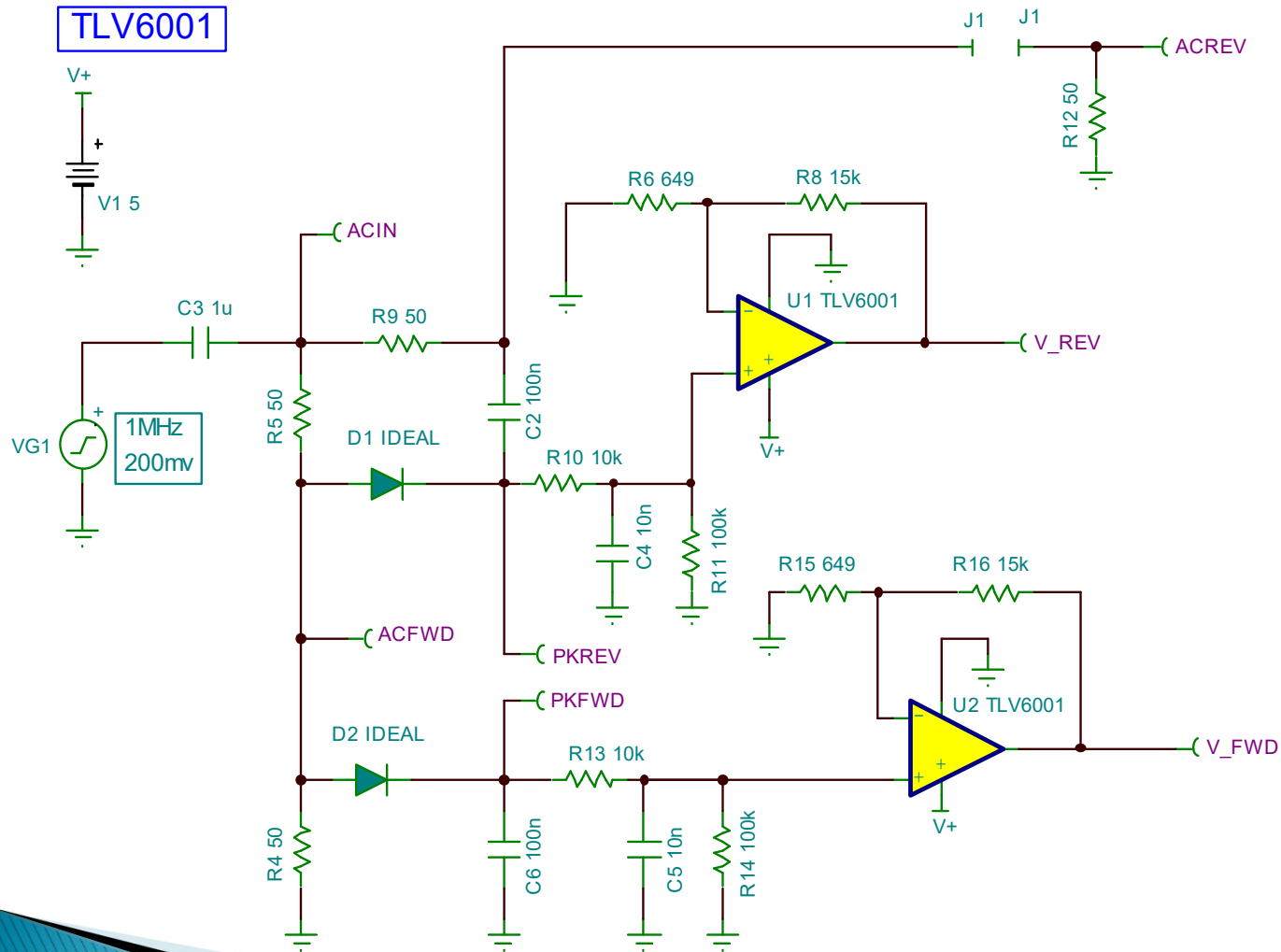


Settling Time - 1N34A

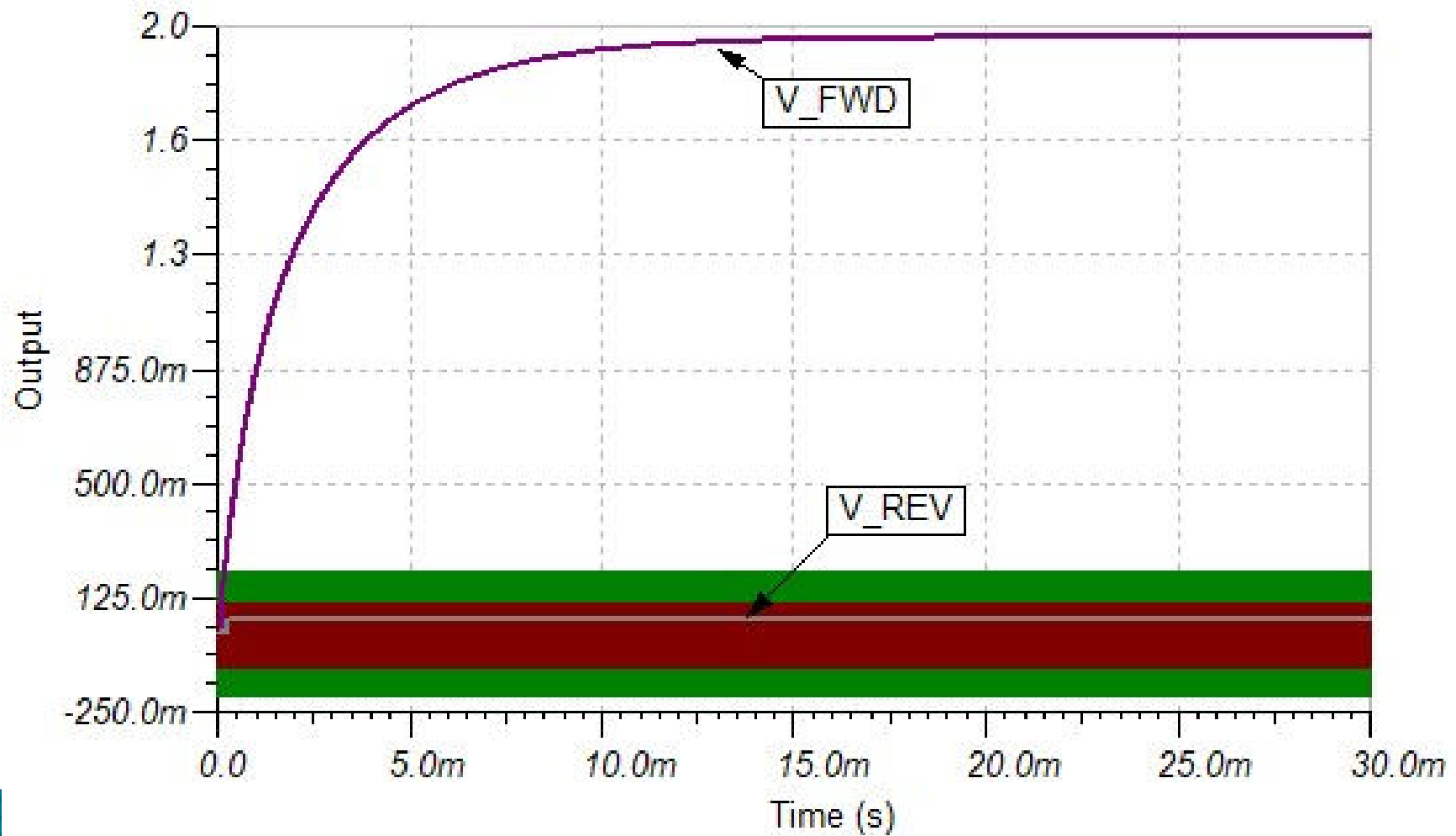


Ideal Diodes vs. Theory

Case: Reference Design Simulated with ideal diodes

Zo =	50 ohms		AA1		
			ideal		
Load	Vrev	Vfwd	diodes	lamda	theory
4	1.840	2.166	12.289	-0.852	12.50
6	1.696	2.168	8.199	-0.786	8.33
10	1.438	2.170	4.930	-0.667	5.00
15	1.161	2.173	3.294	-0.538	3.33
20	0.924	2.176	2.478	-0.429	2.50
25	0.720	2.178	1.987	-0.333	2.00
30	0.540	2.179	1.660	-0.250	1.67
40	0.247	2.177	1.256	-0.111	1.25
50	0.023	2.191	1.021	0.000	1.00
55	0.107	2.184	1.103	0.048	1.10
60	0.206	2.191	1.208	0.091	1.20
70	0.370	2.192	1.406	0.167	1.40
100	0.727	2.189	1.995	0.333	2.00
130	0.965	2.192	2.573	0.444	2.60
150	1.084	2.187	2.964	0.500	3.00
200	1.297	2.187	3.915	0.600	4.00
250	1.439	2.188	4.846	0.667	5.00
300	1.541	2.188	5.764	0.714	6.00
350	1.617	2.191	6.628	0.750	7.00
400	1.676	2.191	7.504	0.778	8.00
450	1.724	2.188	8.425	0.800	9.00
500	1.762	2.188	9.282	0.818	10.00
550	1.794	2.189	10.101	0.833	11.00
600	1.822	2.188	10.956	0.846	12.00

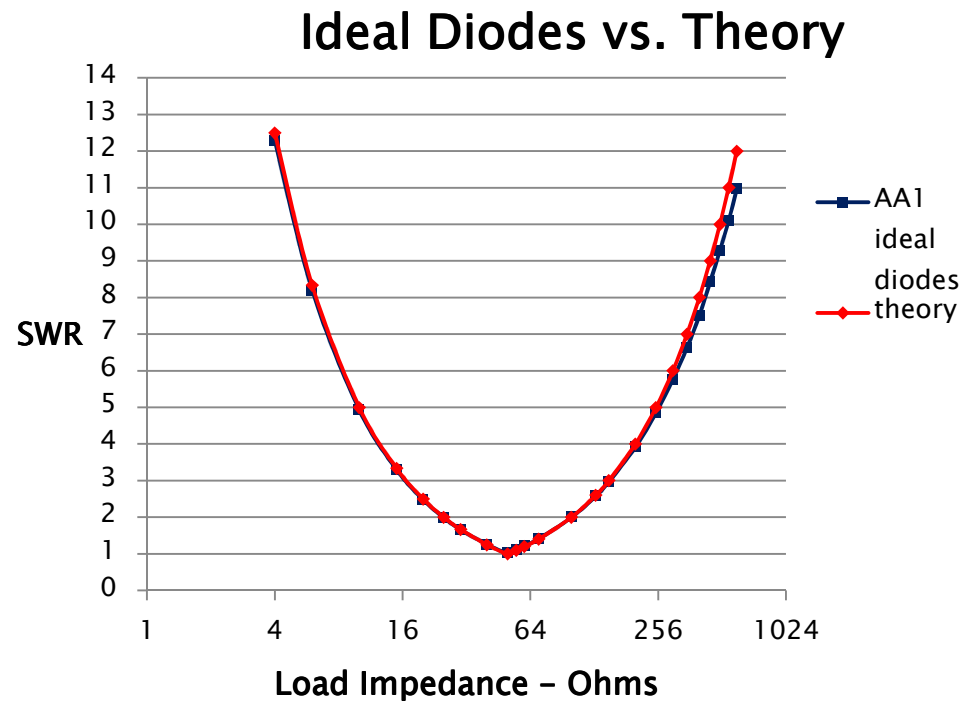


Ideal Diodes vs. Theory

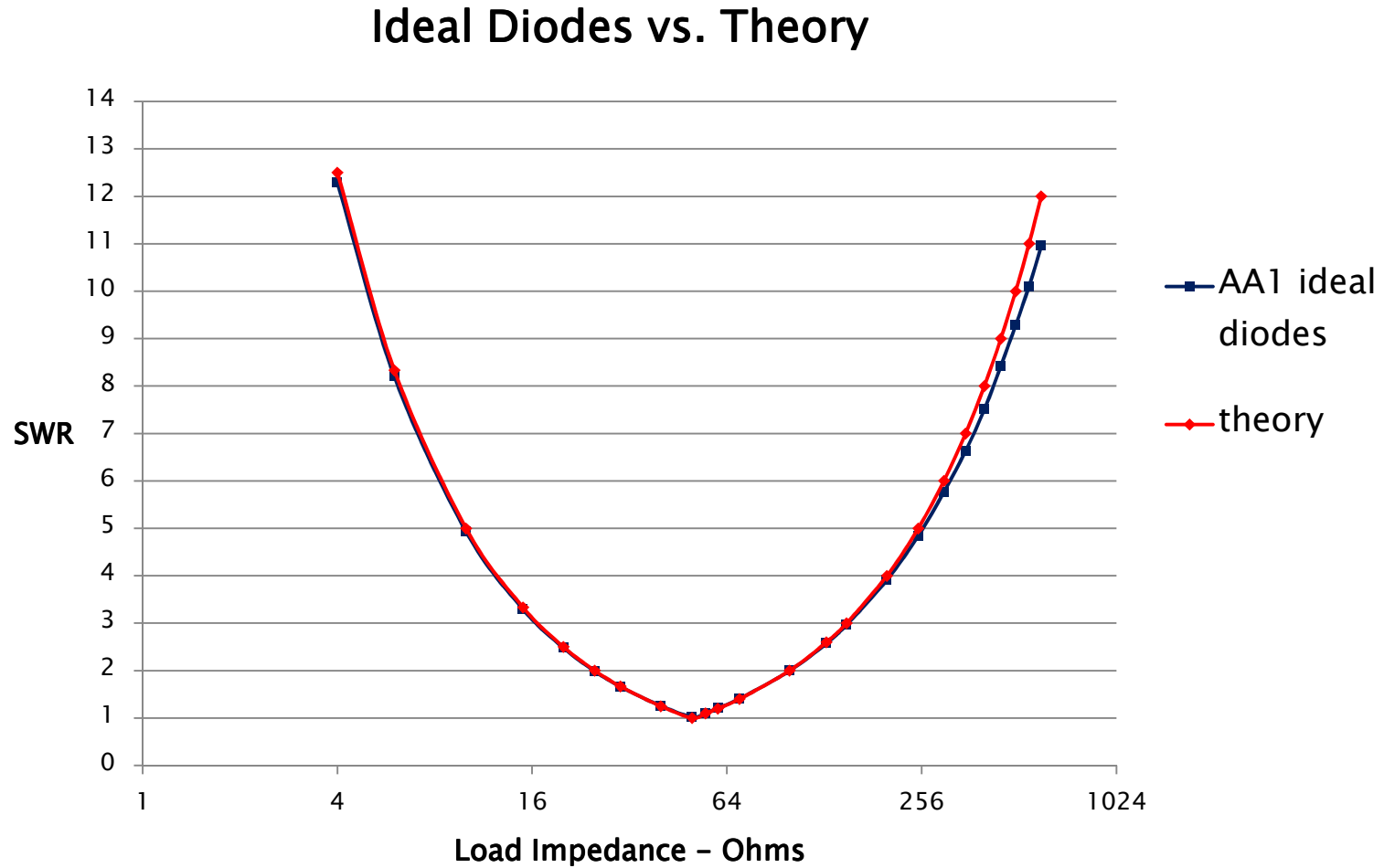


Germanium Diodes vs. Theory

1N34A vs. Theory

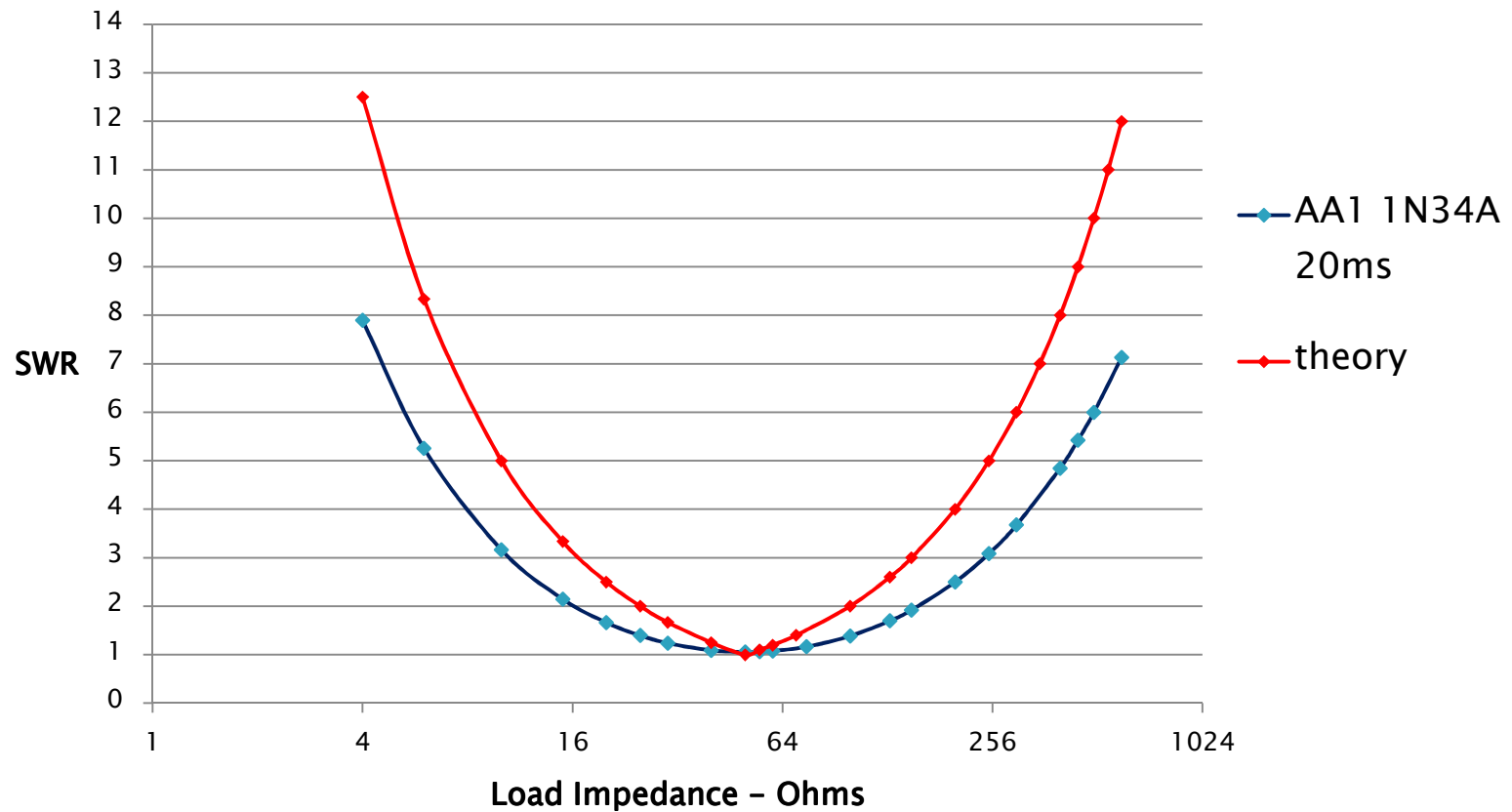

Schottky Diodes vs. Theory


Schottky Diodes vs. Theory

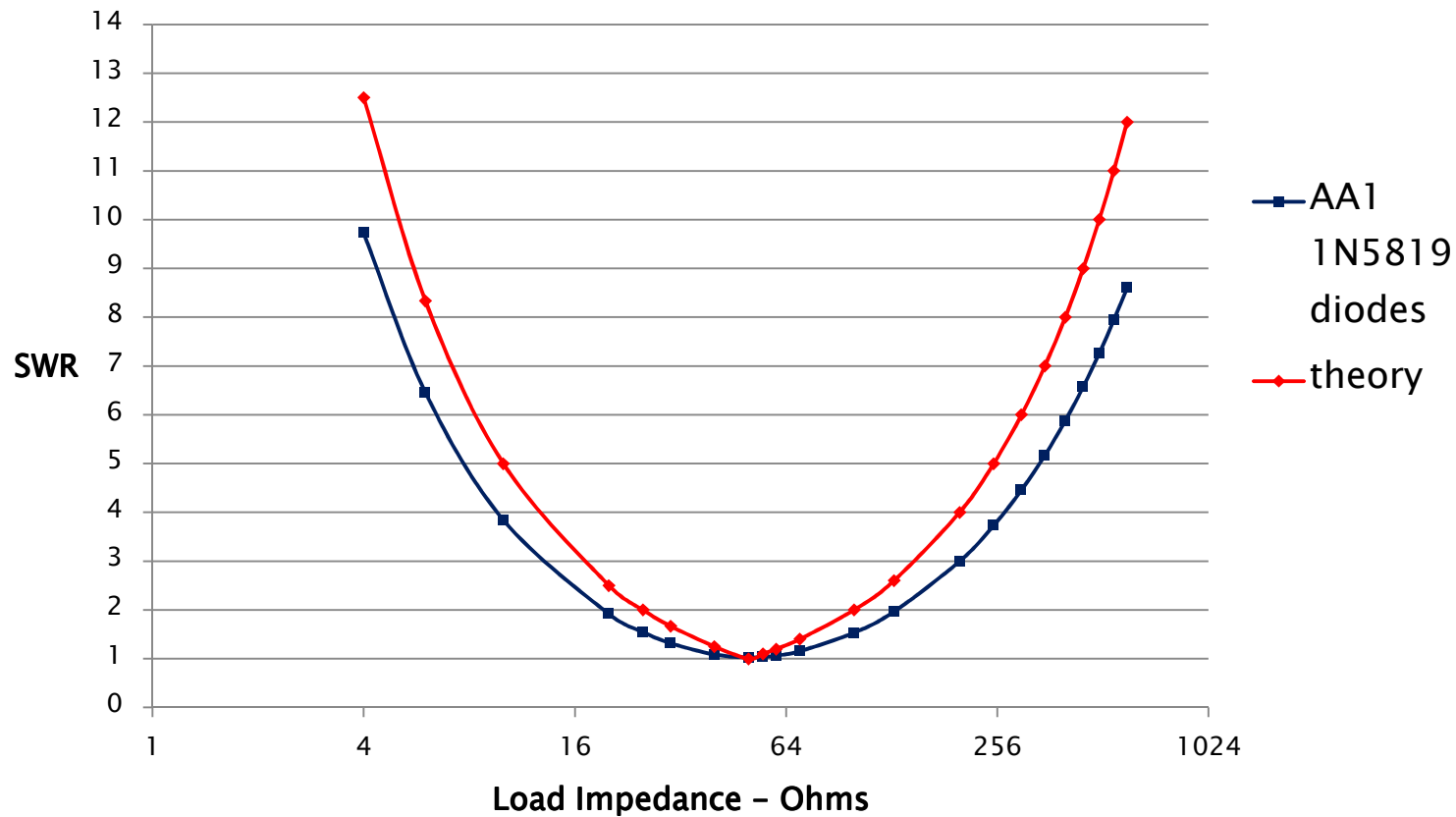


Op Amp Peak Detector

Barry Basile, 8/30/17
SWR Meter


OPA2355

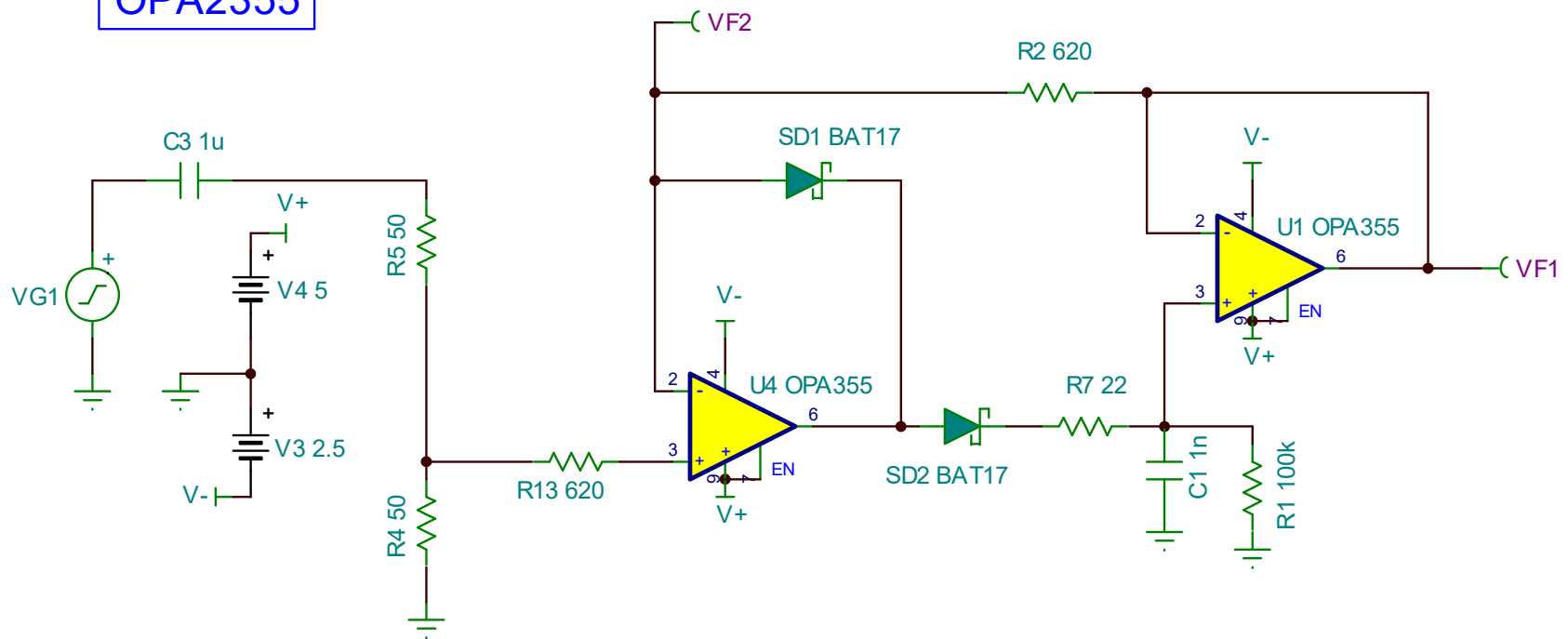

Op Amp Peak Detector

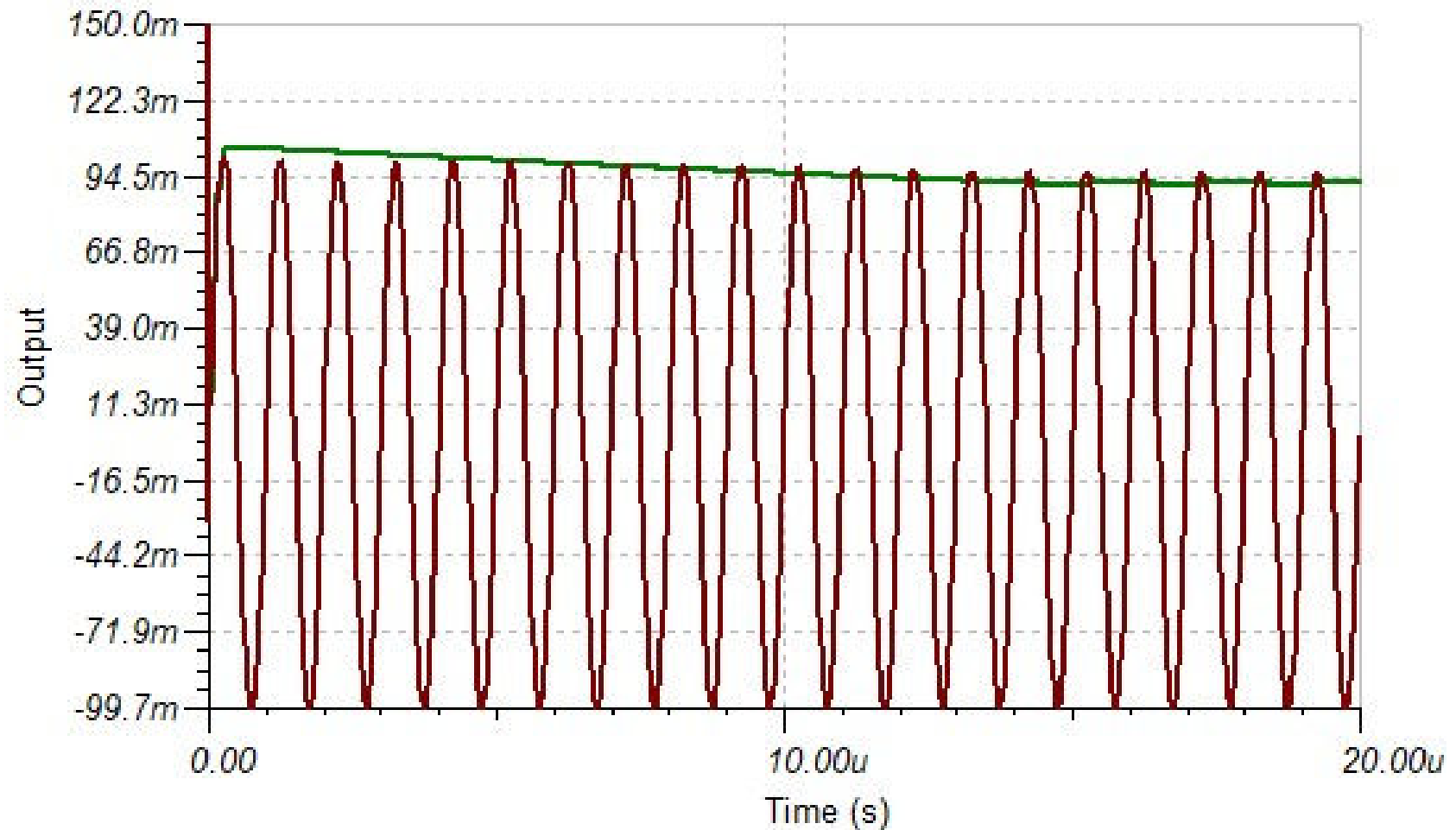


Op Amp Peak Detector

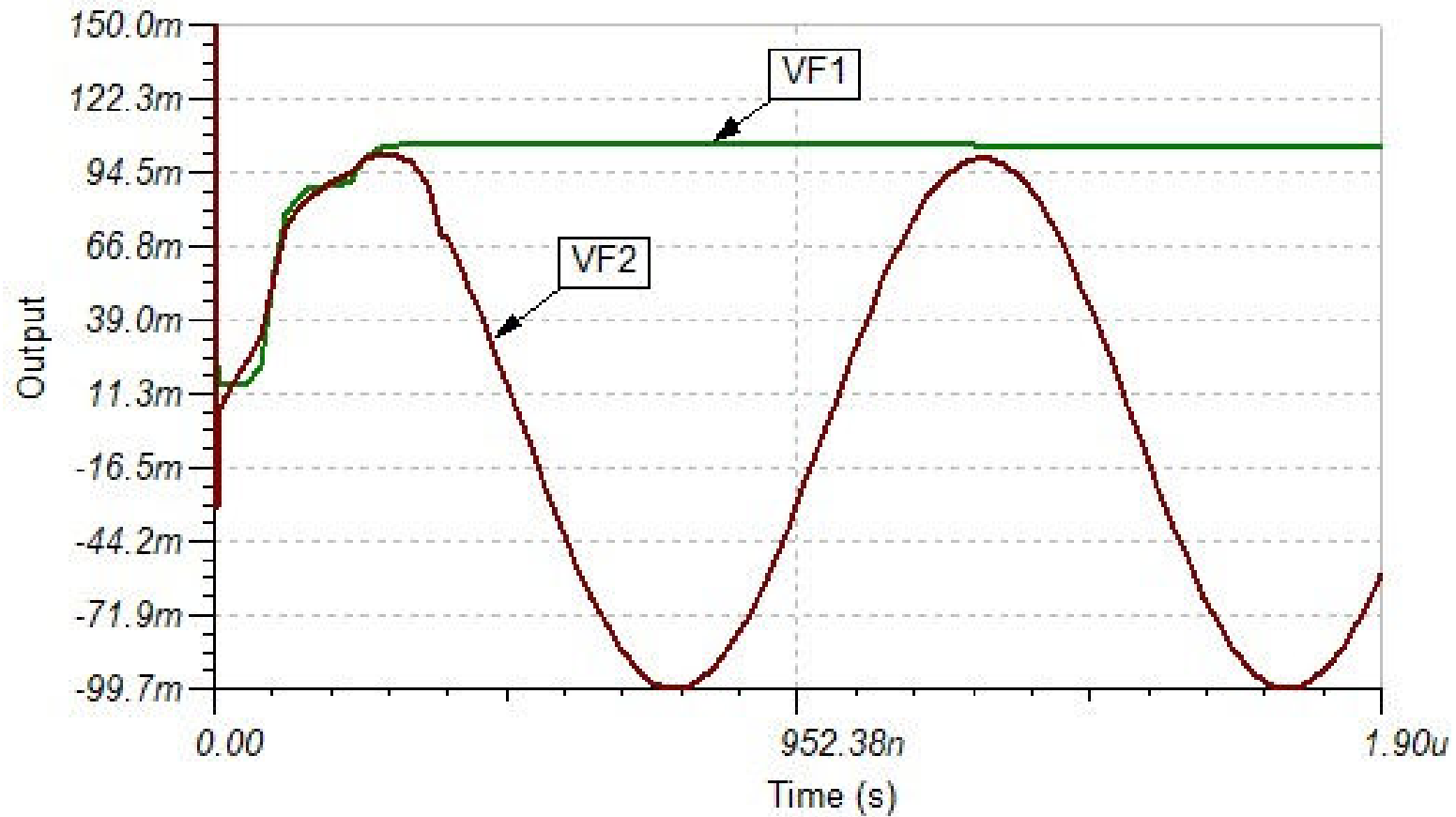

Best Solution – Use LTC5507

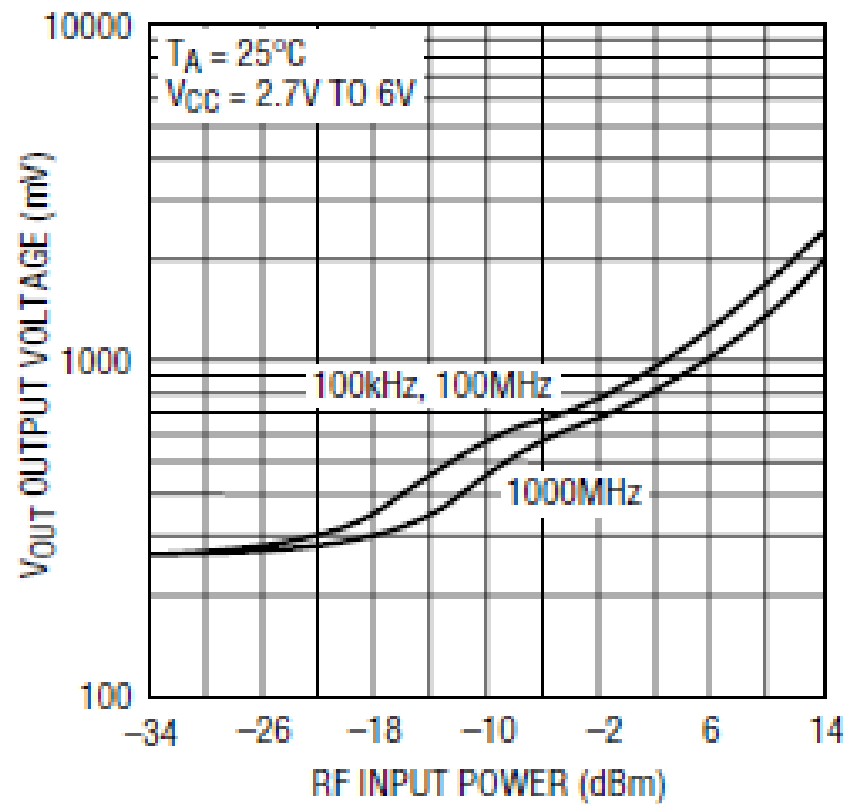Typical Detector Characteristics
at 100kHz, 100MHz and 1000MHz



5507 TA01b

Future Plans

- ▶ Build and test original design with various diodes and measure accuracy against fixed dummy loads
- ▶ Develop an enhanced version using LTC5507 in place of diodes
- ▶ Report results to the club!



References

Original Description by K6BEZ:

www.hamstack.com/hs_projects/k6bez_antenna_analyzer.pdf

Wheatstone Bridge:

<http://www.electronics-tutorials.ws/blog/wheatstone-bridge.html>

VI Curves:

<http://www.electronics-tutorials.ws/blog/i-v-characteristic-curves.html>

Maximum Power Transfer:

https://en.wikipedia.org/wiki/Maximum_power_transfer_theorem

SPICE:

<https://en.wikipedia.org/wiki/SPICE>

TINA:

https://e2e.ti.com/support/development_tools/webench_design_center/b/elabblog/archives/2011/05/03/download-tina-ti-version-9-1

Diode SPICE models:

http://www.keysight.com/upload/cmc_upload/All/Diode.pdf

